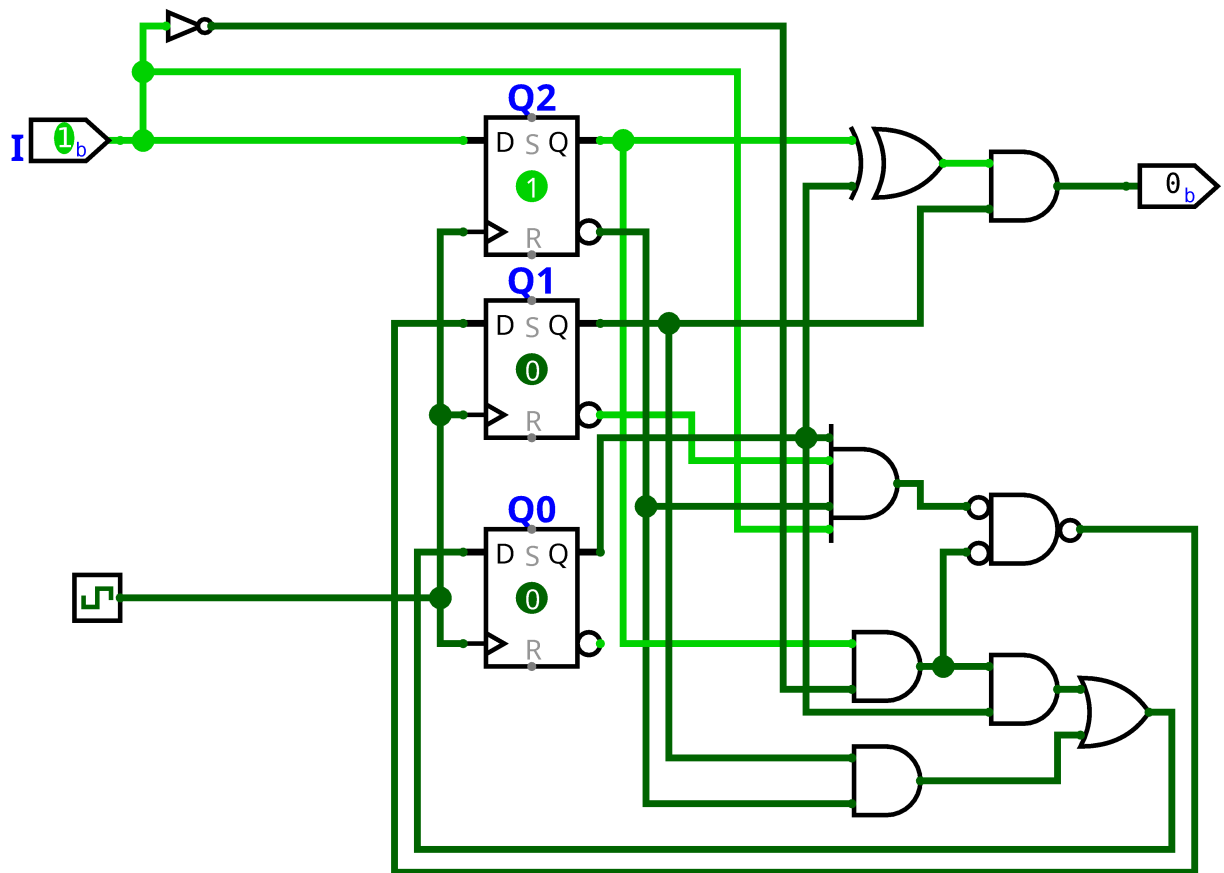



Lab 7 - More Sequential Circuit Analysis & Design

- Objective:
 - Design and simulate a sequential logic circuit using flip-flops
 - Analyze the logic diagram of a sequence detector and determine:
 - Mealy or Moore device
 - What is the code sequence
 - What are the timing characteristics
 - Design & implement a sequence detector that detects two sequences
 - UNLOCK should be asserted for whenever the last four inputs are either:
 - 1101
 - 1010
 - Include:
 - State diagram
 - State table
 - Boolean equations
 - Labeled logic diagram
 - Design the circuit as both a Moore and Mealy device
 - Analyze advantages/disadvantages of each device:
 - Hardware requirements
 - Memory
 - Timing
 - Security
 - Ease of design
- Figure #1 Circuit Diagram Analysis

- Circuit Diagram:




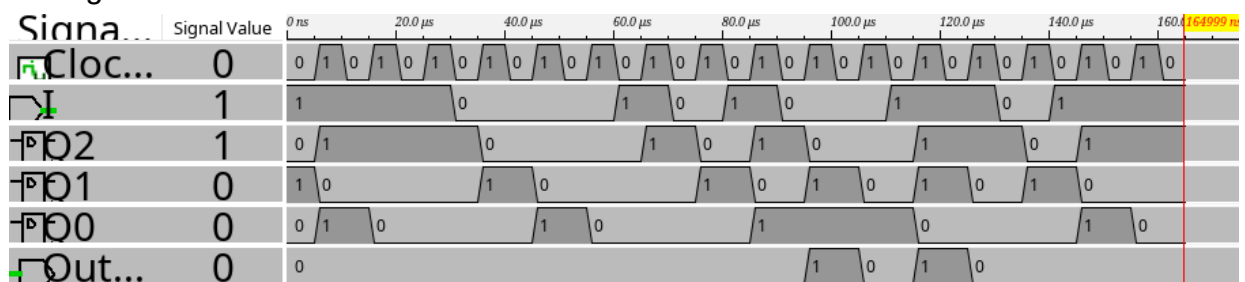- This circuit is a Moore device, as the input does not directly affect the status of the output
- The code sequence for unlocking this circuit appears to be 1010
- Timing characteristics:




- Sequence detector:

- Moore Implementation:

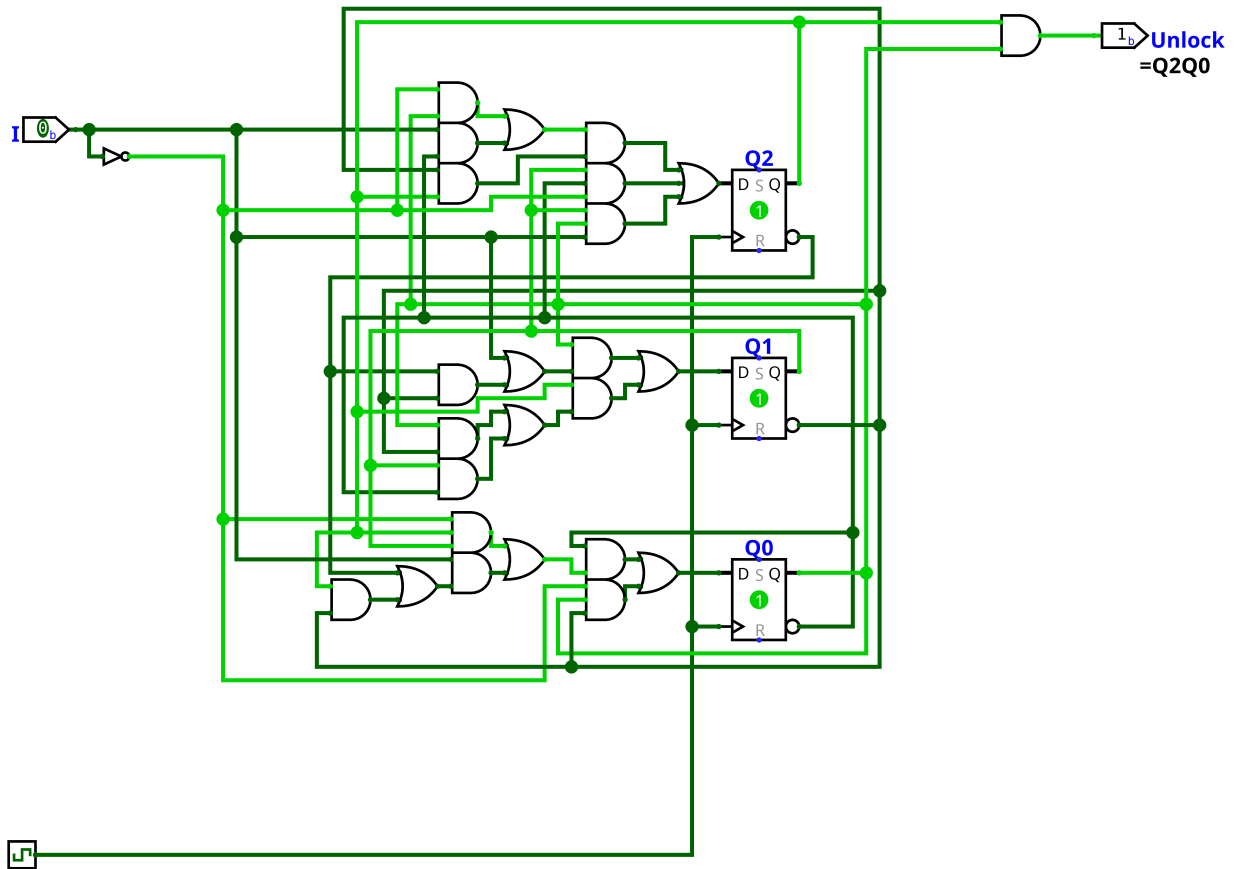


- See attached PDF of hand notes

- Timing Diagram:

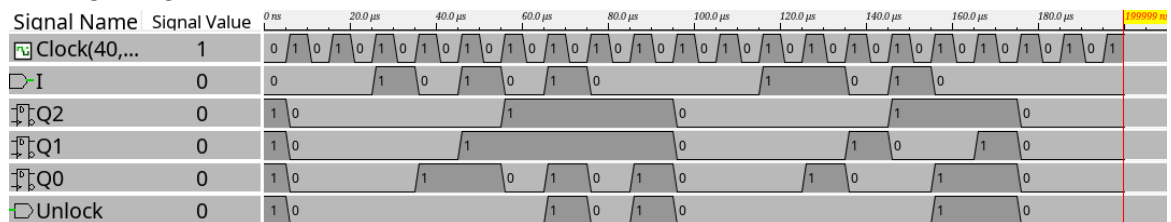


- Mealy Implementation:
- See attached

• Version 1:

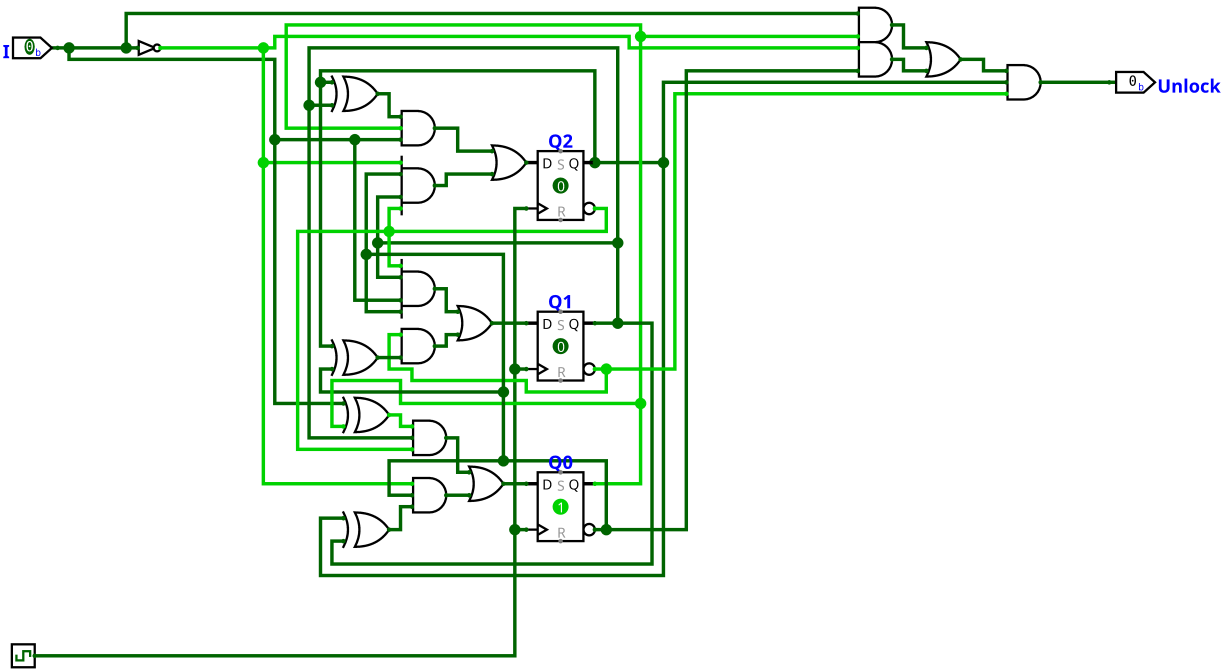

• Version 2:

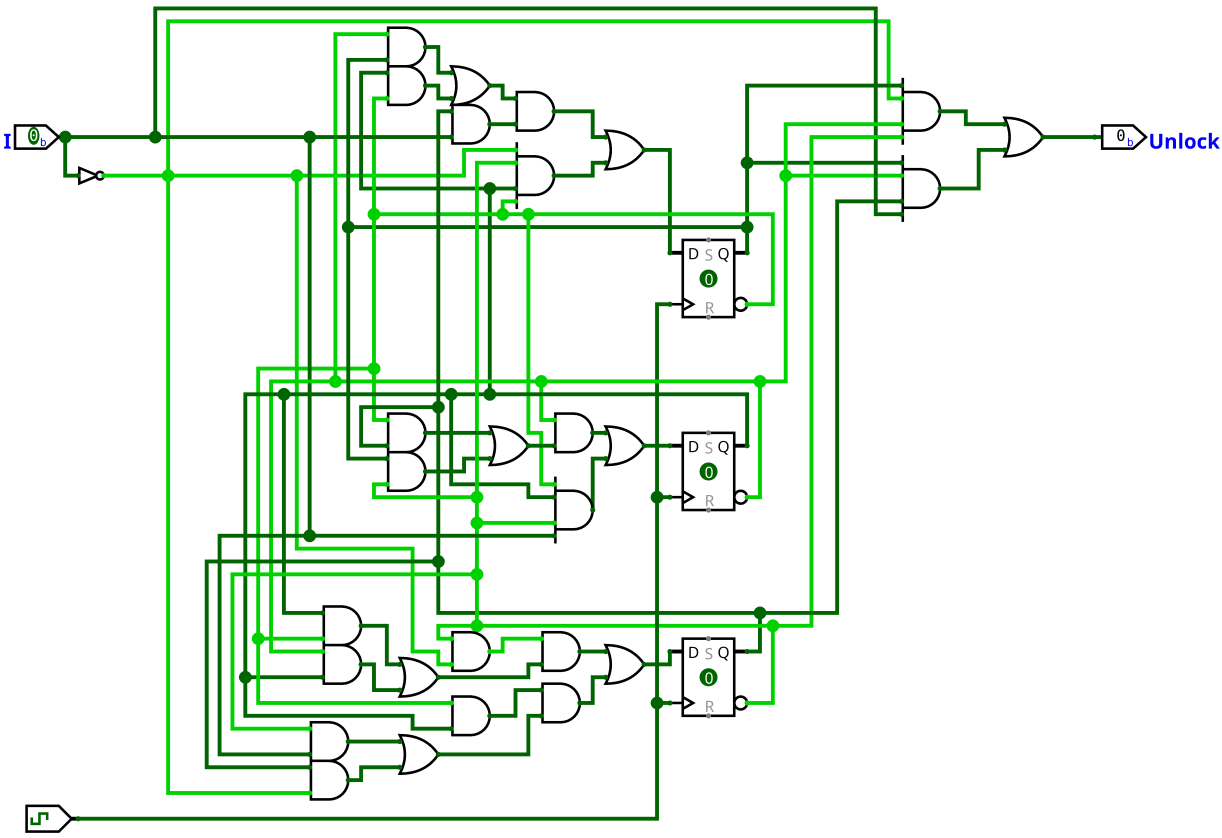

• Timing Diagram for version 1 implementation:

